Ejercicio 1:

Puerta xor

```
E124.0 E124.1 ()

E124.0 E124.1
```

Biestable: RS→SR

A124.1

E124.2 "q"

"s1"

SR


"q"

()


E124.3

"r"-R

Biestable 2: SR→ RS

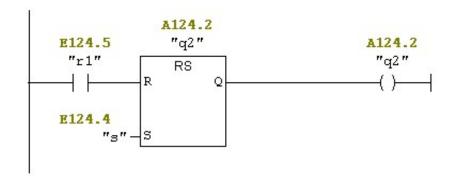

Ejercicio 2:

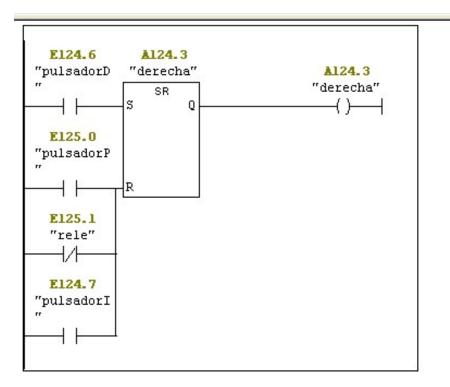

Segm. 5: Título:

```
Comentario:
```

